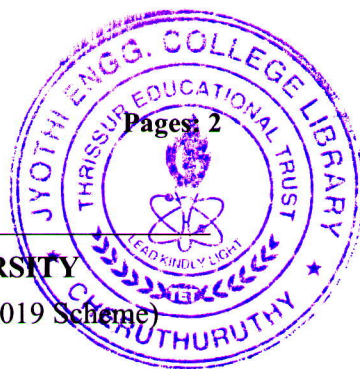


C

0800CST203122001



Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

Third Semester B.Tech Degree Examination December 2020 (2019 Scheme)

Course Code: CST203

Course Name: LOGIC SYSTEM DESIGN

Max. Marks: 100

Duration: 3 Hours

## PART A

*Answer all questions. Each question carries 3 marks*

Marks

- 1 Convert  $(456.78)_{10}$  to a) binary b) octal and c) hexadecimal (3)
- 2 Write a) 1's complement and 2) 2's complement representations of  $(-126)$  (3)
- 3 State and prove De Morgan's Theorem (3)
- 4 Design a circuit using NAND gates for implementing EXCLUSIVE-OR function (3)
- 5 Design a half adder circuit using any universal gate. (3)
- 6 Draw the logic diagram of a  $2 \times 1$  multiplexer circuit (3)
- 7 Derive the characteristic equation of a D flip flop from its excitation table. (3)
- 8 How is a sequential circuit different from a combinational circuit? Give an example for each circuit. (3)
- 9 Distinguish between a ring counter and Johnson counter (3)
- 10 When do you implement a combinational circuit using ROM and when do you implement a combinational circuit using PLA in preference to ROM. (3)

## PART B

*Answer any one full question from each module. Each question carries 14 marks*

## Module 1

- 11 a) Convert i)  $(13AF)_{16}$  to octal ii)  $(10110101.101)_2$  to decimal (6)
- b) Add i) BCD numbers 1567 and 968 ii) octal numbers 2376 and 5677 (8)
- 12 a) Perform the following operations using 2's complement representation (10)
  - i)  $(-34) + (+21)$  ii)  $(+26) - (-12)$  iii)  $(-33) + (-22)$  iv)  $(+45) - (+32)$
- b) Convert i)  $(10011010)$  in 2's complement form to decimal (4)
- ii)  $(10111001)$  in 1's complement form to decimal

## Module 2

- 13 a) Using K Map simplify the function (8)
 
$$F(w, x, y, z) = \sum (0, 1, 2, 3, 5, 7, 8, 9, 10, 13, 15)$$
- b) Express the above function in product of maxterms form. (6)

- 14 a) Using tabulation method simplify the function (8)

$$F(w,x,y,z) = \sum (0,2,4,5,6,7,8,12,13,14,15)$$

- b) Express the following functions in a canonical form (6)

i)  $F = D + BC'$  ii)  $F = AB' + BC'$

**Module 3**

- 15 a) Design a full subtractor circuit. (6)

- b) Design a code converter for converting a BCD to excess-3 code. (8)

- 16 a) Explain BCD adder using a block diagram. (7)

- b) Design a 2 bit magnitude comparator. (7)

**Module 4**

- 17 a) With a logic diagram explain how a master slave flip flop overcomes race around problem. (7)

- b) Design a 2 bit synchronous counter. (7)

- 18 a) Draw the state diagram and logic diagram of a BCD ripple counter. (6)

- b) Design a 3 bit synchronous up-down counter. (8)

**Module 5**

- 19 a) Explain the working of a 3 stage Johnson ring counter with a block diagram (7)

- b) Explain the working of a 3 bit bidirectional shift register with parallel load. (7)

- 20 a) Illustrate the algorithm for addition and subtraction of two floating point numbers. (7)

- b) Illustrate the algorithm for addition and subtraction two binary numbers in sign magnitude form. (7)

\*\*\*\*\*