



# KTU NOTES

The learning companion.

**KTU STUDY MATERIALS | SYLLABUS | LIVE  
NOTIFICATIONS | SOLVED QUESTION PAPERS**

<b>Module: 3</b>	<b>ARITHMETIC ALGORITHMS</b> - Algorithms for multiplication and division (restoring method) of binary numbers — Array multiplier —Booth's multiplication algorithm <b>Pipelining</b> - Basic Principles, classification of pipeline processors. instruction and arithmetic pipelines (Design examples not required), hazard detection and resolution.
------------------	---

## MULTIPLICATION OF UNSIGNED NUMBERS

Product of 2 n bit numbers is atmost 2n bit number. Unsigned multiplication can be viewed as addition of shifted versions of the multiplicand. Multiplication involves the generation of partial products, one for each digit in the multiplier. These partial products are then summed to produce the final product. When the multiplier bit is 0, the partial product is 0. When the multiplier is 1 the partial product is the multiplicand. The total product is produced by summing the partial products. For this operation, each successive partial product is shifted one position to the left relative to the preceding partial product.

Multiplication of two integer numbers 13 and 11 is,


$$\begin{array}{r}
 \begin{array}{r}
 1101 \\
 \times 1011 \\
 \hline
 1101 \\
 11010 \\
 00000 \\
 110100 \\
 \hline
 10001111
 \end{array}
 \end{array}
 \begin{array}{l}
 (13) \text{ Multiplicand M} \\
 (11) \text{ Multiplier Q} \\
 \\
 \\
 \\
 (143) \text{ Product P}
 \end{array}$$

(a) Manual multiplication algorithm

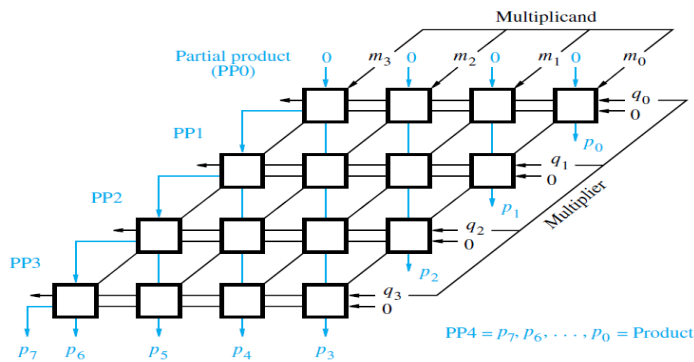
### Array Multiplier

Binary multiplication can be implemented in a combinational two-dimensional logic array called **array multiplier**.

- The main component in each in each cell is a full adder, FA.
- The AND gate in each cell determines whether a multiplicand bit  $m_j$ , is added to the incoming partial product bit based on the value of the multiplier bit,  $q_i$ .
- Each row  $i$ , where  $0 \leq i \leq 3$ , adds the multiplicand (appropriately shifted) to the incoming parcel product,  $PP_i$ , to generate the outgoing partial product,  $PP(i+1)$ , if  $q_i=1$ .
- If  $q_i=0$ ,  $PP_i$  is passed vertically downward unchanged.  $PP_0$  is all 0's and  $PP_4$  is the desired product. The multiplication is shifted left one position per row by the diagonal signal path.



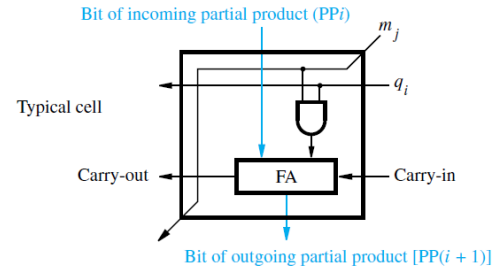(a) Array multiplication of positive binary operands



(b) Multiplier cell

### Disadvantages:

- (1) An  $n$  bit by  $n$  bit array multiplier requires  $n^2$  AND gates and  $n(n-2)$  full adders and  $n$  half adders. (Half adders are used if there are 2 inputs and full adder used if there are 3 inputs).
- (2) The longest part of input to output through  $n$  adders in top row,  $n-1$  adders in the bottom row and  $n-3$  adders in middle row. The longest in a circuit is called **critical path**.

### Sequential Circuit Multiplier


Multiplication is performed as a series of  $(n)$  conditional addition and shift operation such that if the given bit of the multiplier is 0 then only a shift operation is performed, while if the given bit of the multiplier is 1 then addition of the partial products and a shift operation are performed.

The combinational array multiplier uses a large number of logic gates for multiplying numbers. Multiplication of two  $n$ -bit numbers can also be performed in a sequential circuit that uses a single  $n$  bit adder.

The block diagram in Figure shows the **hardware arrangement for sequential multiplication**. This circuit performs multiplication by using single  $n$ -bit adder  $n$  times to implement the spatial addition performed by the  $n$  rows of ripple-carry adders in Figure. Registers A and Q are shift registers, concatenated as shown. Together, they hold partial product  $PP_i$  while multiplier bit  $q_i$  generates the signal Add/Noadd. This signal causes the multiplexer MUX to select 0 when  $q_i = 0$ , or to select the multiplicand  $M$  when  $q_i = 1$ , to be added to  $PP_i$  to generate  $PP(i+1)$ . The product is computed in  $n$  cycles. The partial product grows in length by one bit per cycle from the initial vector,  $PP_0$ , of  $n$  0s in register A. The carryout from the adder is stored in flipflop C, shown at the left end of the register C.

### Algorithm:

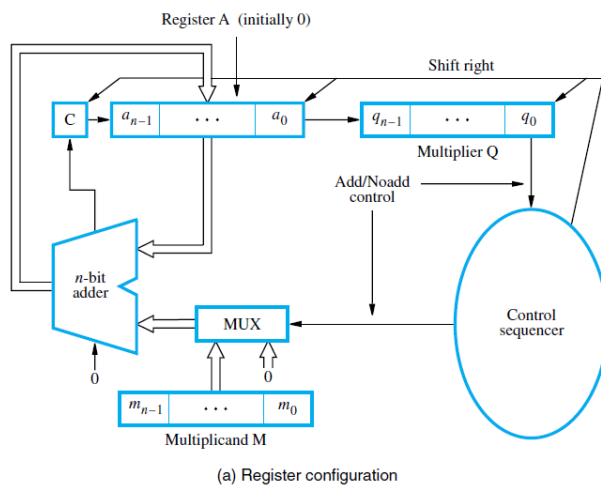- (1) The multiplier and multiplicand are loaded into two registers Q and M. Third register A and C are cleared to 0.
- (2) In each cycle it performs 2 steps:
  - (a) If LSB of the multiplier  $q_i = 1$ , control sequencer generates **Add** signal which adds the multiplicand M with the register A and the result is stored in A.
  - (b) If  $q_i = 0$ , it generates **Noadd** signal to restore the previous value in register A.
- (3) Right shift the registers C, A and Q by 1 bit



	M				
	1 1 0 1				
0	0 0 0 0				1 0 1 1
C	A				Q
0	1 1 0 1				1 0 1 1
0	0 1 1 0				1 1 0 1
1	0 0 1 1				1 1 0 1
0	1 0 0 1				1 1 1 0
0	1 0 0 1				1 1 1 0
0	0 1 0 0				1 1 1 1
1	0 0 0 1				1 1 1 1
0	1 0 0 0				1 1 1 1
	Product				

(b) Multiplication example

## MULTIPLICATION OF SIGNED NUMBERS

We now discuss multiplication of 2's-complement operands, generating a **double-length** product. The general strategy is still to accumulate partial products by adding versions of the multiplicand as selected by the multiplier bits.

First, consider the case of a **positive multiplier and a negative multiplicand**. When we add a negative multiplicand to a partial product, we must **extend the sign-bit value** of the multiplicand to the **left** as far as the product will extend. Figure shows an example in which a 5-bit signed operand, -13, is the multiplicand. It is multiplied by +11 to get the 10-bit product, -143. The sign extension of the multiplicand is shown in blue. The hardware discussed earlier can be used for negative multiplicands if it is augmented to provide for sign extension of the partial products.

$$\begin{array}{rcl}
 13 & \rightarrow & 1101 \\
 +13 & \rightarrow & 01101 \quad [\text{for +ve number, add 0 to MSB}] \\
 -13 & \rightarrow & 10010 + \quad [\text{for -ve number, find 2's complement}] \\
 & & 1 \\
 \hline
 & & 10011 \rightarrow -13
 \end{array}$$

[To extend the sign bit - since its 5 bit signed operand, 10 bit product should be generated.  
So, if the partial product's MSB is 1, add 1 for sign extension (to left),  
if the partial product's MSB is 0, add 0 for sign extension (to left)]

**Example:** Sign extension of negative multiplicand

					1	0	0	1	1	(-13)
					×	0	1	0	1	(+11)
Sign extension is shown in blue										
1	1	1	1	1	1	1	0	0	1	1
1	1	1	1	1	1	0	0	1	1	
0	0	0	0	0	0	0	0	0		
1	1	1	0	0	1	1				
0	0	0	0	0	0					
1	1	0	1	1	1	0	0	0	1	(-143)

[product is 10 bits  $\rightarrow (2n)$ ]

For a **negative multiplier**, a straightforward solution is to form the **2's-complement of both the multiplier and the multiplicand** and proceed as in the case of a positive multiplier. This is possible because complementation of both operands does not change the value or the sign of the product.


*[If the sign bit is 0 then the number is positive, If the sign bit is 1, then the number is negative]*

### The Booth Algorithm

#### Algorithm & Flowchart for Booth Multiplication

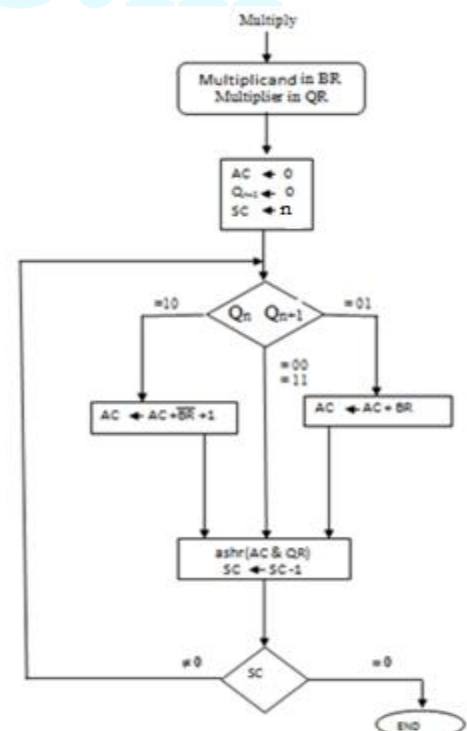1. Multiplicand is placed in BR and Multiplier in QR
2. Accumulator register AC,  $Q_{n+1}$  are initialized to 0
3. Sequence counter SC is initialized to n (number of bits).
4. Compare  $Q_n$  and  $Q_{n+1}$  and perform the following
  - 01  $\rightarrow AC = AC + BR$
  - 10  $\rightarrow AC = AC + BR' + 1$
  - 00  $\rightarrow$  No arithmetic operation
  - 11  $\rightarrow$  No arithmetic operation
5. ASHR- Arithmetic Shift right AC, QR
6. Decrement SC by 1

The final product will be store in AC, QR



### Multiply -9 x -13 using Booth Algorithm

9 = 1001  
 +9 = 01001  
 -9 = 10110+  
 1

-----  
**10111 (BR)**

13 = 1101  
 +13 = 01101  
 -13 = 100010+  
 1

-----  
**10011 (Q)**

BR= 10111  
 BR'+1= 01000+  
 1  
 -----  
**01001 (BR'+1)**

Q <sub>n</sub>	Q <sub>n+1</sub>	BR=10111	AC	Q	Q <sub>n+1</sub>	SC
		BR'+1=01001				
		Initial	00000	1001 <b>1</b>	<b>0</b>	101
1	0	SUB	00000+			
			01001			
			01001	10011	0	101
		ASHR	<b>0</b> 0100	1100 <b>1</b>	<b>1</b>	100
1	1	ASHR	<b>0</b> 0010	0110 <b>0</b>	<b>1</b>	011
0	1	ADD	00010+			
			10111			
			11001	01100	1	011
		ASHR	<b>1</b> 1100	1011 <b>0</b>	<b>0</b>	010
0	0	ASHR	<b>1</b> 1110	0101 <b>1</b>	<b>0</b>	001
1	0	SUB	11110			
			01001			
			00111	01011	0	001
		ASHR	<b>0</b> 0011	10101	1	000

**Resultant Product in A and Q = 00011 10101**  
 $= 2^6 + 2^5 + 2^4 + 2^2 + 2^0$   
**= 117**

=====

### Multiply 13 x -6 using Booth Algorithm

13 = 1101  
+13 = **01101 (BR)**

6 = 0110  
+6 = 00110  
-6 = 11001+  
1  
-----  
**11010 (Q)**

BR= 01101  
BR'+1= 10010+  
1  
-----  
**10011 (BR'+1)**

Q <sub>n</sub>	Q <sub>n+1</sub>	BR=01101 BR'+1=10011	AC	Q	Q <sub>n+1</sub>	SC
		Initial	00000	1101 <b>0</b>	<b>0</b>	101
0	0	ASHR	<b>0</b> 0000	0110 <b>1</b>	<b>0</b>	100
1	0	SUB	00000+			
			10011			
			10011	01101	0	100
		ASHR	<b>1</b> 1001	1011 <b>0</b>	<b>1</b>	011
0	1	ADD	11001+			
			01101			
			00110	10110	1	011
		ASHR	<b>0</b> 0011	0101 <b>1</b>	<b>0</b>	010
1	0	SUB	00011			
			10011			
			10110	01011	0	010
		ASHR	<b>1</b> 1011	0010 <b>1</b>	<b>1</b>	001
1	1	ASHR	<b>1</b> 1101	10010	1	000

[13x-6 will give a -ve product. so the resultant product's 2's complement should be determined]

**Resultant Product in A and Q = 11101 10010**

2's complement = 00010 01101+  
1

$$\begin{aligned}
 & \text{-----} \\
 & 0001001110 \\
 & = 2^6 + 2^3 + 2^2 + 2^1 \\
 & \therefore = \mathbf{-78} \\
 & \text{=====}
 \end{aligned}$$

### Multiply -11 x 8 using Booth Algorithm

11 = 1011  
 +11 = 01011  
 -11 = 10100+  
 1  
 -----

**10101 (BR)**

8 = 1000  
 +8 = **01000 (Q)**  
 -

BR= 10101  
 BR'+1= 01010+  
 1  
 -----  
**01011 (BR'+1)**

Q <sub>n</sub>	Q <sub>n+1</sub>	BR=10101	AC	Q	Q <sub>n+1</sub>	SC
		BR'+1=01011				
		Initial	00000	0100 <b>0</b>	<b>0</b>	101
0	0	ASHR	<b>0</b> 0000	0010 <b>0</b>	<b>0</b>	100
0	0	ASHR	<b>0</b> 0000	0001 <b>0</b>	<b>0</b>	011
0	0	ASHR	<b>0</b> 0000	0000 <b>1</b>	<b>0</b>	010
1	0	SUB	00000+			
			01011			
			01011	00001	0	010
		ASHR	<b>0</b> 0101	1000 <b>0</b>	<b>1</b>	001
0	1	ADD	00101			
			10101			
			11010	10000	1	010
		ASHR	<b>1</b> 1101	01000	0	000

[-11x8 will give a -ve product. so the resultant product's 2's compliment should be determined]

### Resultant Product in A and Q = 11101 01000

2's complement = 00010 10111+  
 1

-----  
 0001011000  
 =2<sup>6</sup>+2<sup>4</sup>+2<sup>3</sup>  
 = **-88**  
 =====



**Multiply each of the following pairs of signed 2's complement number using Booth's algorithm. In each of the cases assume A is the multiplicand and B is the multiplier.**

**A=010111 B=110110**

**Answer:**

A=**0**10111

[sign bit is 0, therefore +ve number]

A=23 [10111]

**Therefore, A=+23 [010111]**

B=**1**10110

[sign bit is 1, therefore -ve number]

Find 2's complement.

2's complement of 10110 is 01001+ 1  
= 01010 => 10

**Therefore, B= -10 [110110]**

**Multiply +23 x -10**

+23 = **010111** (BR)

-10 = **110110** (Q)

BR= 010111

BR'+1= 101000+

1

-----  
**101001 (BR'+1)**

Q <sub>n</sub>	Q <sub>n+1</sub>	BR=010111	AC	Q	Q <sub>n+1</sub>	SC
		BR'+1=101001				
		Initial	000000	11011 <b>0</b>	<b>0</b>	0110
0	0	ASHR	<b>0</b> 00000	01101 <b>1</b>	<b>0</b>	0101
1	0	SUB	000000+			
			101001			
			101001	011011	0	0101
		ASHR	<b>1</b> 10100	10110 <b>1</b>	<b>1</b>	0100
1	1	ASHR	<b>1</b> 11010	01011 <b>0</b>	<b>1</b>	0011
0	1	ADD	111010+			
			010111			
			010001	010110	1	0011
		ASHR	<b>0</b> 01000	10101 <b>1</b>	<b>0</b>	0010
1	0	SUB	001000+			
			101001			
			110001	101011	0	0010
		ASHR	<b>1</b> 11000	11010 <b>1</b>	<b>1</b>	0001
1	1	ASHR	<b>1</b> 11100	01101 <b>0</b>	<b>1</b>	0000

[+23x-10 will give a -ve product. so the resultant product's 2's compliment should be determined]

**Resultant Product in A and Q = 111100 011010**

2's complement = 000011 100101+

1

-----  
000011100110

$= 2^7 + 2^6 + 2^5 + 2^2 + 2^1$

**= -230**

=====

### **Features of Booth Algorithm:**

- Booth algorithm works equally well for both negative and positive multipliers.
- Booth algorithm deals with signed multiplication of given number.
- Speed up the multiplication process.

### **Booth Recording of a Multiplier:**

In general, in the Booth algorithm,  $-1$  times the shifted multiplicand is selected when moving from 0 to 1, and  $+1$  times the shifted multiplicand is selected when moving from 1 to 0, as the multiplier is scanned from right to left. The case when the LSB of the multiplier is 1, it is handled by assuming that an implied 0 lies to its right.

Multiplier		Version of multiplicand selected by bit $i$	Example																	
Bit $i$	Bit $i-1$		0	0	1	0	1	1	0	0	1	1	1	0	1	0	1	1	0	
0	0	$0 \times M$																		
0	1	$+1 \times M$	0	+1	-1	+1	0	-1	0	+1	0	0	-1	+1	-1	+1	0	-1	0	
1	0	$-1 \times M$																		
1	1	$0 \times M$																		

Booth recoding of a multiplier.

- In worst case multiplier, numbers of addition and subtraction operations are large.
- In ordinary multiplier, 0 indicates no operation, but still there are addition and subtraction operations to be performed.
- In good multiplier, booth algorithm works well because majority are 0s .
- A good multiplier consists of block/sequence of 1s.

Worst-case multiplier	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
	+1	-1	+1	-1	+1	-1	+1	-1	+1	-1	+1	-1	+1	-1	+1	-1
Ordinary multiplier	1	1	0	0	0	1	0	1	1	0	1	1	1	1	0	0
	0	-1	0	0	+1	-1	+1	0	-1	+1	0	0	0	-1	0	0
Good multiplier	0	0	0	0	1	1	1	1	1	0	0	0	0	1	1	1
	0	0	0	+1	0	0	0	0	-1	0	0	0	+1	0	0	-1

Booth recoded multipliers.

Booth algorithm achieves efficiency in the number of additions required when the multiplier had a **few large blocks of 1s**. The speed gained by skipping over 1s depends on the data. On average, the speed of doing multiplication with the booth algorithm is the same as with the normal multiplication

- Best case – a long string of 1's (skipping over 1s)
- Worst case – 0's and 1's are alternating
- The transformation 011....110 to 100....0-10 is called **skipping over 1s**.

## INTEGER DIVISION

Figure shows examples of decimal division and binary division of the same values. Consider the decimal version first. The 2 in the quotient is determined by the following reasoning: First, we try to divide 13 into 2, and it does not work. Next, we try to divide 13 into 27. We go through the trial exercise of multiplying 13 by 2 to get 26, and, observing that  $27 - 26 = 1$  is less than 13, we enter 2 as the quotient and perform the required subtraction.

$$\begin{array}{r} 21 \\ 13 \overline{) 274} \\ \underline{26} \phantom{0} \\ 14 \phantom{0} \\ \underline{13} \phantom{0} \\ 1 \phantom{0} \end{array}$$

$$\begin{array}{r} 10101 \\ 1101 \overline{) 100010010} \\ \underline{1101} \phantom{000} \\ 10000 \phantom{0} \\ \underline{1101} \phantom{00} \\ 1110 \phantom{0} \\ \underline{1101} \phantom{0} \\ 1 \phantom{0} \end{array}$$

Dividend = 274

Divisor = 13

Quotient=21

Remainder =1

The next digit of the dividend, 4, is brought down, and we finish by deciding that 13 goes into 14 once and the remainder is 1. We can discuss binary division in a similar way, with the simplification that the only possibilities for the quotient bits are 0 and 1.

A circuit that implements division by this longhand method operates as follows: It positions the divisor appropriately with respect to the dividend and performs a subtraction. If the remainder is zero or positive, a quotient bit of 1 is determined, the remainder is extended by another bit of the dividend, the divisor is repositioned, and another subtraction is performed.

If the remainder is negative, a quotient bit of 0 is determined, the dividend is restored by adding back the divisor, and the divisor is repositioned for another subtraction. This is called the **restoring division algorithm**.

### Restoring Division

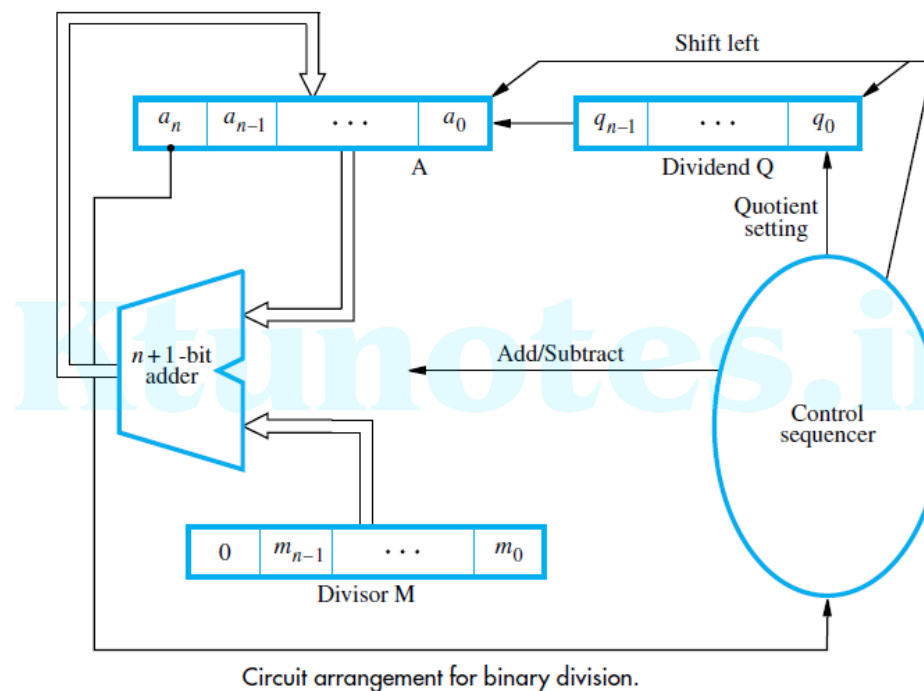


Figure shows a logic circuit arrangement that implements the restoring division algorithm just discussed. An  $n$ -bit positive **divisor** is loaded into register **M** and an  $n$ -bit positive **dividend** is loaded into register **Q** at the start of the operation. Register **A** is set to **0**. After the division is complete, the  $n$ -bit **quotient** is in register **Q** and the **remainder** is in register **A**.

The required subtractions are facilitated by using 2's-complement arithmetic. The extra bit position at the left end of both A and M accommodates the sign bit during subtractions. The following algorithm performs restoring division.

Do the following three steps n times:

1. Shift A and Q left one bit position.
2. Subtract M from A, ie; (A-M) and place the answer back in A.
3. If the sign of A is 1, set  $q_0$  to 0 and add M back to A (that is, restore A); otherwise, set  $q_0$  to 1.

$$\begin{array}{r}
 10 \\
 11 \overline{) 1000} \quad Q \\
 \underline{11} \phantom{00} \\
 10
 \end{array}$$

$$M = 00011$$

$$M' + 1 = 11100 + 1$$

$$= 11101$$

Initially	0 0 0 0 0 A	1 0 0 0 Q	
	0 0 0 1 1 M		
Shift A, Q	0 0 0 0 1 A	0 0 0 0 Q	
Subtract	1 1 1 0 1 M'+1		q <sub>0</sub>
Set q <sub>0</sub>	1 1 1 1 0 A		
Restore	0 0 0 1 1 M		
	0 0 0 0 1 A	0 0 0 0 Q	
Shift A, Q	0 0 0 1 0 A	0 0 0 0 Q	
Subtract	1 1 1 0 1 M'+1		
Set q <sub>0</sub>	1 1 1 1 1 A		
Restore	0 0 0 1 1 M		
	0 0 0 1 0 A	0 0 0 0 Q	
Shift A, Q	0 0 1 0 0 A	0 0 0 0 Q	
Subtract	1 1 1 0 1 M'+1		
Set q <sub>0</sub>	0 0 0 0 1 A		
		0 0 0 1 Q	
Shift A, Q	0 0 0 1 0 A	0 0 1 0 Q	
Subtract	1 1 1 0 1 M'+1		
Set q <sub>0</sub>	1 1 1 1 1 A		
Restore	0 0 0 1 1 M		
	0 0 0 1 0 A	0 0 1 0 Q	

A restoring division example.

$$\text{Dividend} = 8 [1000], \quad \text{Divisor} = 3 [11]$$

$$\text{Quotient} = 2 [0010], \quad \text{Remainder} = 2 [00010]$$

## PIPELINING

Pipelining is a technique of decomposing a sequential process into sub operations, with each sub process being executed in a special dedicated segment that operates concurrently with all other segments. A pipeline can be visualized as a collection of processing segments through which binary information flows. Each segment performs partial processing dictated by the way the task is partitioned. The result obtained from the computation in each segment is transferred to the next segment in the pipeline. The final result is obtained after the data have passed through all segments.

A pipeline processor may process each instruction in 4 steps:


**F Fetch:** Read the instruction from the memory

**D Decode:** Decode the instruction and fetch the source operands


**E Execute:** Perform the operation specified by the instruction

**W Write:** Store the result in the destination location.

In figure (a) four instructions progress at any given time. This means that four distinct hardware units are needed as in figure (b). These units must be capable of performing their tasks simultaneously without interfering with one another. Information is passed from one unit to next through a storage buffer. As an instruction progresses through the pipeline, all the information needed by the stages downstream must be passed along.

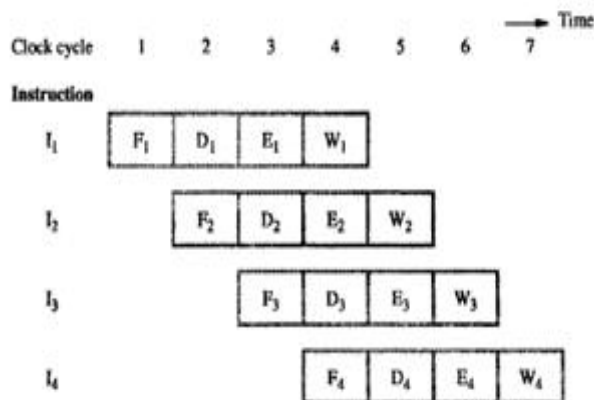

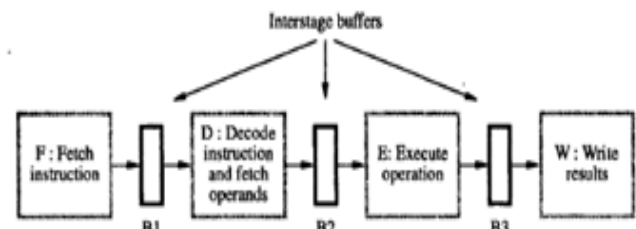(a) Instruction execution divided into four steps



(b) Hardware organization

## Pipeline Organization

The simplest way of viewing the pipeline structure is to imagine that each segment consists of an input register followed by a combinational circuit. The register holds the data and the combinational circuit performs the sub operation in the particular segment. The output of the combinational circuit is applied to the input register of the next segment. A clock is applied to all registers after enough time has elapsed to perform all segment activity. In this way the information flows through the pipeline one step at a time. Example demonstrating the pipeline organization

Suppose we want to perform the combined multiply and add operations with a stream of numbers.

$$A_i * B_i + C_i \quad \text{for } i=1, 2, 3 \dots 7$$

Each sub operation is implemented in a segment within a pipeline. Each segment has one or two registers and a combinational circuit as shown in fig.


R1 through R5 are registers that receive new data with every clock pulse.

The multiplier and adder are combinational circuits.

The sub operations performed in each segment of the pipeline are as follows:

$R1 \leftarrow A_i$	$R2 \leftarrow B_i$	Input $A_i$ and $B_i$
$R3 \leftarrow R1 * R2$	$R4 \leftarrow C_i$	multiply and input $C_i$
$R5 \leftarrow R3 + R4$		add $C_i$ to product

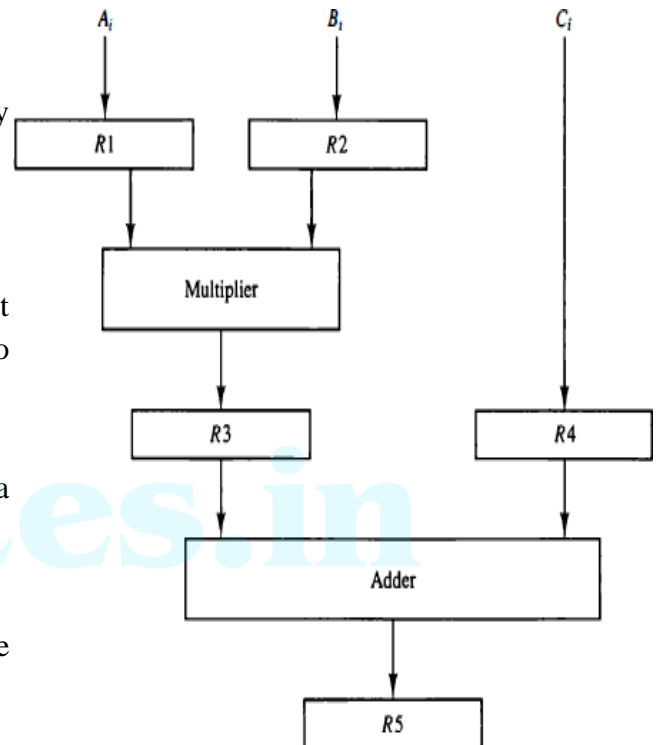The five registers are loaded with new data every clock pulse.




Clock Pulse Number	Segment 1		Segment 2		Segment 3
	R1	R2	R3	R4	R5
1	$A_1$	$B_1$	—	—	—
2	$A_2$	$B_2$	$A_1 * B_1$	$C_1$	—
3	$A_3$	$B_3$	$A_2 * B_2$	$C_2$	$A_1 * B_1 + C_1$
4	$A_4$	$B_4$	$A_3 * B_3$	$C_3$	$A_2 * B_2 + C_2$
5	$A_5$	$B_5$	$A_4 * B_4$	$C_4$	$A_3 * B_3 + C_3$
6	$A_6$	$B_6$	$A_5 * B_5$	$C_5$	$A_4 * B_4 + C_4$
7	$A_7$	$B_7$	$A_6 * B_6$	$C_6$	$A_5 * B_5 + C_5$
8	—	—	$A_7 * B_7$	$C_7$	$A_6 * B_6 + C_6$
9	—	—	—	—	$A_7 * B_7 + C_7$

The first clock pulse transfers A1 and B1 into R1 and R2. The second clock pulse transfers the product of R1 and R2 into R3 and C1 into R4. The same clock pulse transfers A2 and B2 into R1 and R2. The third clock pulse operates on all three segments simultaneously. It places A3 and B3 into R1 and R2, transfers the product of R1 and R2 into R3, transfers C2 into R4, and places the sum of R3 and R4 into R5. It takes three clock pulses to fill up the pipe and retrieve the first output from R5. From there on, each clock produces a new output and moves the data one step down the pipeline. This happens as long as new input data flow into the system.
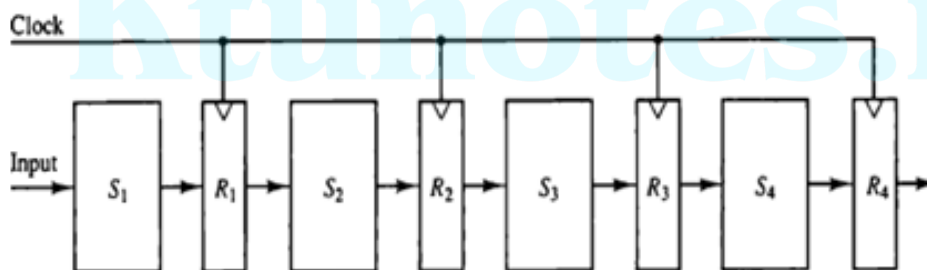
### Four Segment Pipeline

The general structure of four segment pipeline is shown in fig. the operands are passed through all four segments in affixed sequence. Each segment consists of a combinational circuit  $S_i$  that performs a sub operation over the data stream flowing through the pipe. The segments are separated by registers  $R_i$  that hold the intermediate results between the stages. Information flows between adjacent stages under the control of a common clock applied to all the registers simultaneously.




### Space Time Diagram

The behavior of a pipeline can be illustrated with a space time diagram. This is a diagram that shows the segment utilization as a function of time.

Fig - The horizontal axis displays the time in clock cycles and the vertical axis gives the segment number. The diagram shows six tasks T1 through T6 executed in four segments. Initially, task T1 is handled by segment 1. After the first clock, segment 2 is busy with T1, while segment 1 is busy with task T2. Continuing in this manner, the first task T1 is completed after fourth clock cycle. From then, the pipe completes a task every clock cycle.



Consider the case where a k-segment pipeline with a clock cycle time  $t_p$  is used to execute n tasks. The first task  $T_1$  requires a time equal to  $k t_p$  to complete its operation since there are k segments in a pipe. The remaining n-1 tasks emerge from the pipe at the rate of one task per clock cycle and they will be completed after a time equal to  $(n-1) t_p$ . Therefore, to complete n tasks using a k segment pipeline requires  $k + (n-1)$  clock cycles.

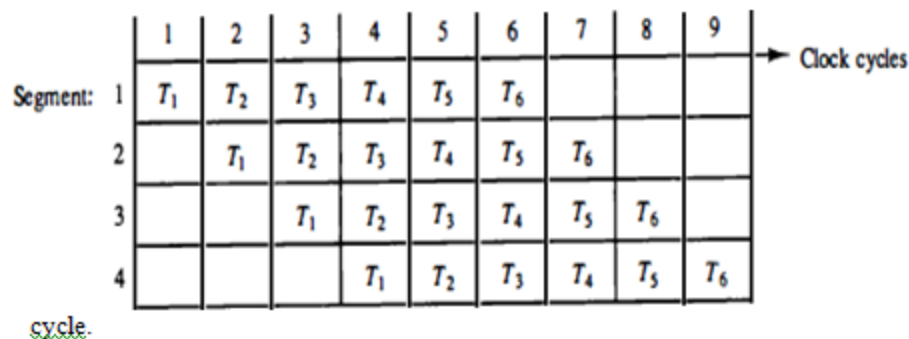

Consider a non pipeline unit that performs the same operation and takes a time equal to  $t_n$  to complete each task. The total time required for n tasks is  $n t_n$ . The speedup of a pipeline processing over an equivalent non pipeline processing is defined by the ratio

$$S = \frac{n t_n}{(k + n - 1) t_p}$$

As the number of tasks increases, n becomes much larger than k-1, and  $k + n - 1$  approaches the value of n. under this condition the speed up ratio becomes

$$S = \frac{t_n}{t_p}$$


If we assume that the time it takes to process a task is the same in the pipeline and non pipeline circuits, we will have  $t_n = k t_p$ . Including this assumption speedup ratio reduces to

$$S = \frac{k t_p}{t_p} = k$$

### CLASSIFICATION OF PIPELINE PROCESSORS

- 1. Arithmetic Pipelining:** The arithmetic logic units of a computer can be segmented for pipeline operations in various data formats.
- 2. Instruction Pieplining:** The execution of stream of instructions can be pipelined by overlapping the execution of current instruction with the fetch, decode and execution of subsequent instructions. This technique is known as **instruction lookahead**.

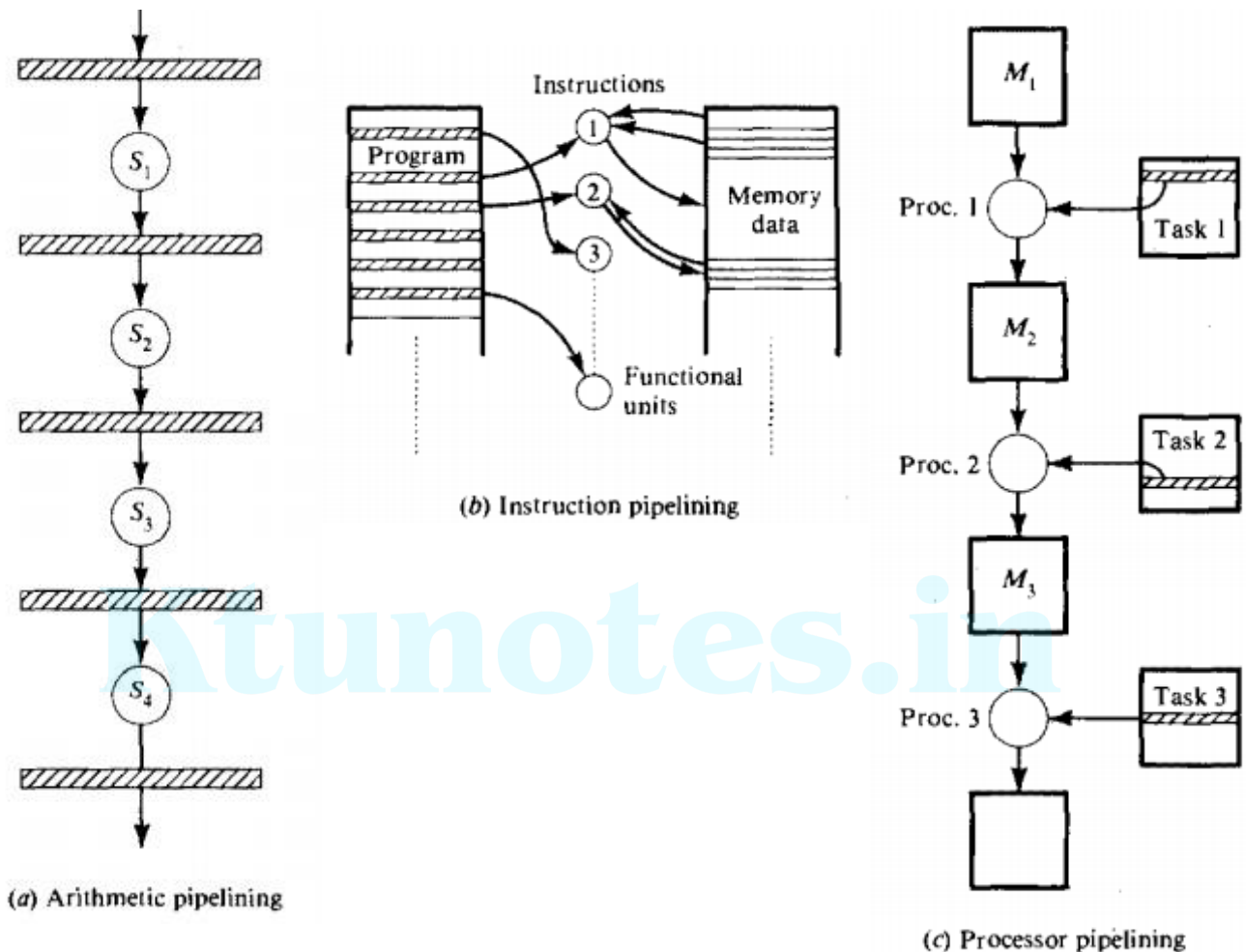- 3. Processor Pipelining:** Pipeline processing of the same data stream by a cascade of processors, each of which processes a specific task. The data stream passes the first processor with the results stored in memory block which is also accessible by the second processor. The second processor then passes the refined results to the third and so on.



### ARITHMETIC PIPELINES


An arithmetic pipeline divides an arithmetic operation into sub operations for execution in the pipeline segments. Pipeline arithmetic units are usually found in very high speed computers. They are used to implement floating point operations, multiplication of fixed point numbers, and similar computations encountered in scientific problems.

**Pipeline Unit For Floating Point Addition And Subtraction:**

The inputs to the floating point adder pipeline are two normalized floating point binary numbers.

$$X = A * 2^a$$

$$Y = B * 2^b$$

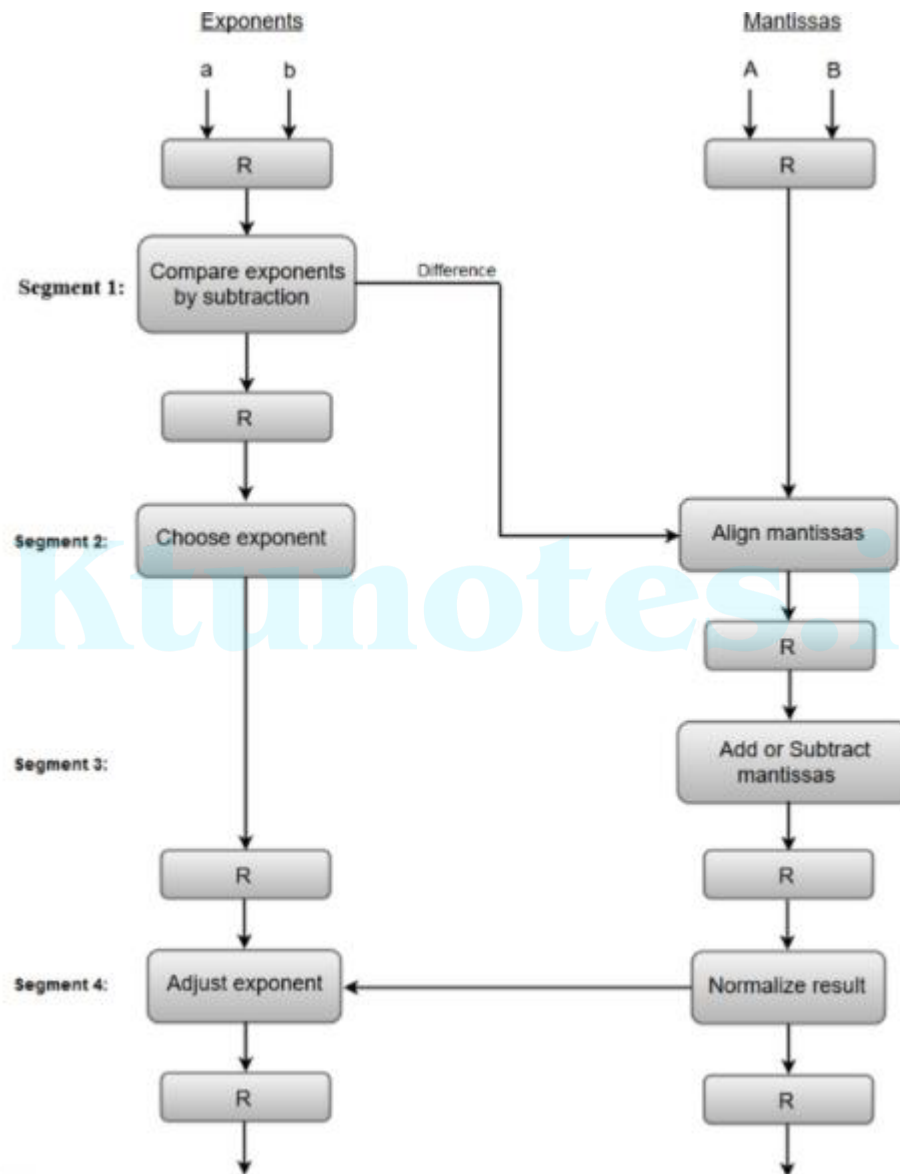

A and B are two fractions that represent the mantissa and a and bare the exponents. The floating point addition and subtraction can be performed in four segments. The registers labeled are placed between the segments to store intermediate results. The sub operations that are performed in the four segments are:

1. Compare the exponents
2. Align the mantissa.
3. Add or subtract the mantissas.
4. Normalize the result.

The exponents are compared by subtracting them to determine their difference. The larger exponent is chosen as the exponent of the result. The exponent difference determines how many times the mantissa associated with the smaller exponent must be shifted to the right. This produces an alignment of the two mantissas.

The two mantissas are added or subtracted in segment 3. The result is normalized in segment 4. When an overflow occurs, the mantissa of the sum or difference is shifted to right and the exponent incremented by one. If the underflow occurs, the number of leading zeroes in the mantissa determines the number of left shifts in the mantissa and the number that must be subtracted from the exponent.

### **INSTRUCTION PIPELINE**

An instruction pipeline operates on a stream of instructions by overlapping the fetch, decode, and execute phases of instruction cycle. An instruction pipeline reads consecutive instructions from memory while previous instructions are being executed in other segments. This causes the instruction fetch and executes phases to overlap and perform simultaneous operations.

Consider a computer with an instruction fetch unit and an instruction execute unit designed to provide a two segment pipeline. The instruction fetch segment can be implemented by means of a first in first out (FIFO) buffer. Whenever the execution unit is not using memory, the control increments the program counter and uses its address value to read consecutive instructions from memory. The instructions are inserted into the FIFO buffer

so that they can be executed on a first in first out basis. Thus an instruction stream can be placed in queue, waiting for decoding and processing by the execution segment.

In general the computer needs to process each instruction with the following sequence of steps.

1. Fetch the instruction.
2. Decode the instruction.
3. Calculate the effective address.
4. Fetch the operands from memory.
5. Execute the instruction.
6. Store the result in the proper place.

#### Four Segment Instruction Pipeline

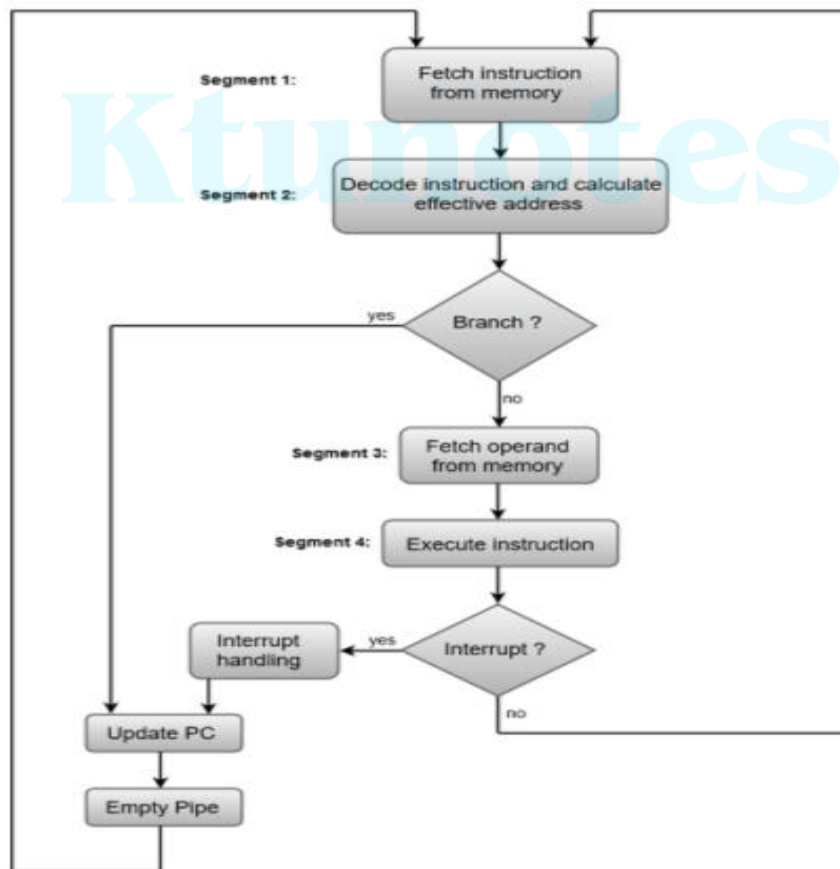


Fig shows the instruction cycle in the CPU can be processed with a four segment pipeline. While an instruction is being executed in segment 4, the next instruction in sequence is busy with fetching an operand from memory in segment 3. the effective address may be calculated in a separate arithmetic circuit for the third instruction, and whenever the memory is available, the fourth and all subsequent instructions are placed in an instruction FIFO.

Fig shows the operation of the instruction pipeline. The time in the horizontal axis is divided into steps of equal duration. The four segments are represented in the diagram with an abbreviated symbol.

Step:	1	2	3	4	5	6	7	8	9	10	11	12	13
Instruction: 1	FI	DA	FO	EX									
2		FI	DA	FO	EX								
(Branch) 3			FI	DA	FO	EX							
4				FI	-	-	FI	DA	FO	EX			
5					-	-	-	FI	DA	FO	EX		
6									FI	DA	FO	EX	
7										FI	DA	FO	EX

1. FI is the segment that fetches an instruction.
2. DA is the segment that decodes the instruction and calculates the effective address.
3. FO is the segment that fetches the operand.
4. EX is the segment that executes the instruction.

It is assumed that the processor has separate instruction and data memories so that the operation in FI and FO can proceed at the same time. In the absence of a branch instruction, each segment operates on different instructions. Thus, in step 4, instruction 1 is being executed in segment EX; the operand for instruction 2 is being fetched into segment FO; instruction 3 is being decoded in segment DA; and instruction 4 is being fetched from memory in segment FI.

Assume now this instruction is a branch instruction. As soon as this instruction is decoded in segment DA in step 4, the transfer from FI to DA of the other instructions are halted until the branch instruction is executed in step 6.

**PIPELINE CONFLICTS:**

1. **RESOURCE CONFLICTS:** They are caused by access to memory by two segments at the same time. Most of these conflicts can be resolved by using separate instruction and data memories.
2. **DATA DEPENDENCY:** these conflicts arise when an instruction depends on the result of a previous instruction, but this result is not yet available.
3. **BRANCH DIFFERENCE:** they arise from branch and other instructions that change the value of PC.

**PIPELINE HAZARDS DETECTION AND RESOLUTION****DATA HAZARDS**

- We must ensure that the results obtained when instructions are executed in a pipelined processor are identical to those obtained when the same instructions are executed sequentially.

- Hazard occurs

$$A \leftarrow 3 + A$$

$$B \leftarrow 4 \times A$$

- No hazard

$$A \leftarrow 5 \times C$$

$$B \leftarrow 20 + C$$

- When two operations depend on each other, they must be executed sequentially in the correct order.

- Another example:

Mul R2, R3, R4

Add R5, R4, R6


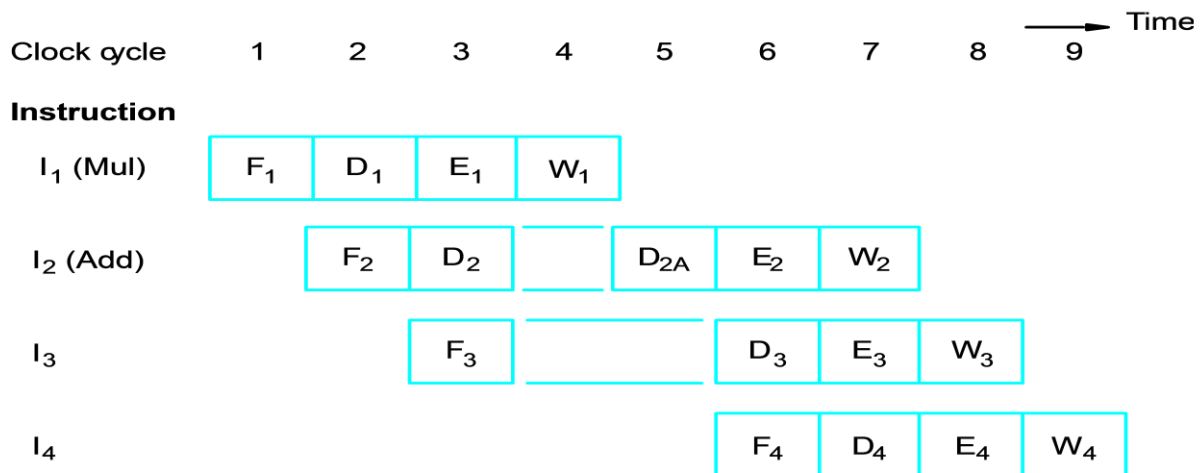


Figure 8.6. Pipeline stalled by data dependency between  $D_2$  and  $W_1$ .

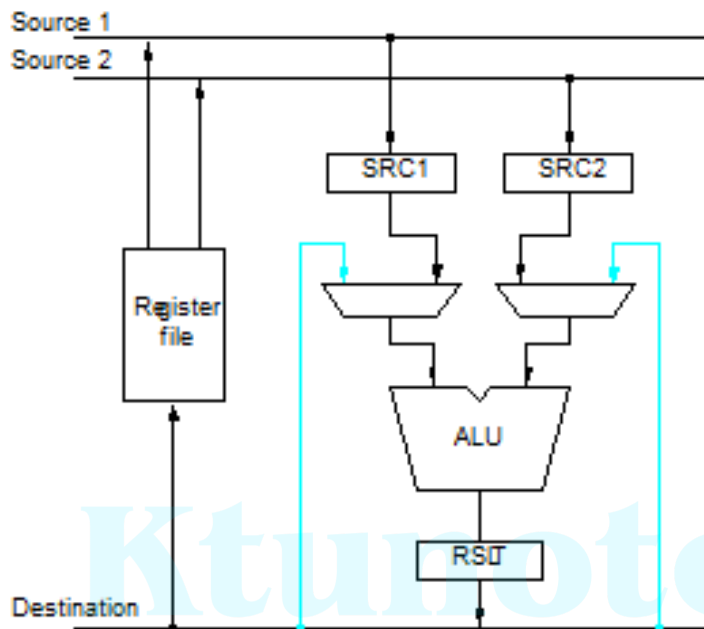


### Operand Forwarding

- Instead of from the register file, the second instruction can get data directly from the output of ALU after the previous instruction is completed.
- A special arrangement needs to be made to “forward” the output of ALU to the input of ALU.



(a) Datapath

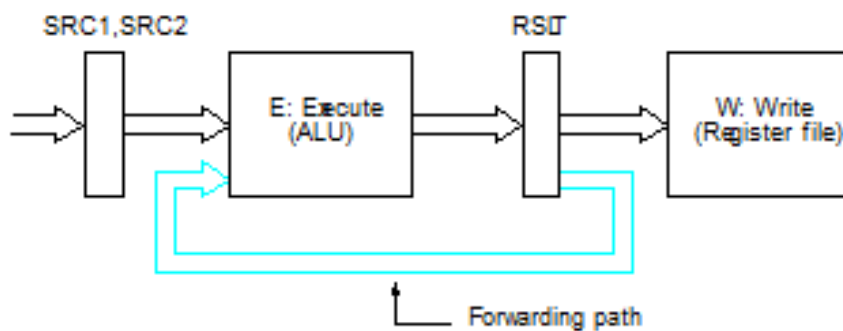

(b) Position of the source and result registers in the processor pipeline

Figure 8.7. Operand forwarding in a pipelined processor

**Handling Data Hazards in Software**

- Let the compiler detect and handle the hazard:

I1: Mul R2, R3, R4

NOP

NOP

I2: Add R5, R4, R6

- The compiler can reorder the instructions to perform some useful work during the NOP slots.

**SIDE EFFECTS**

- The previous example is explicit and easily detected.
- Sometimes an instruction changes the contents of a register other than the one named as the destination.
- When a location other than one explicitly named in an instruction as a destination operand is affected, the instruction is said to have a side effect. (Example?)
- Example: conditional code flags:

Add R1, R3

AddWithCarry R2, R4

- Instructions designed for execution on pipelined hardware should have few side effects.

**INSTRUCTION HAZARDS**

- Whenever the stream of instructions supplied by the instruction fetch unit is interrupted, the pipeline stalls.
- Cache miss
- Branch

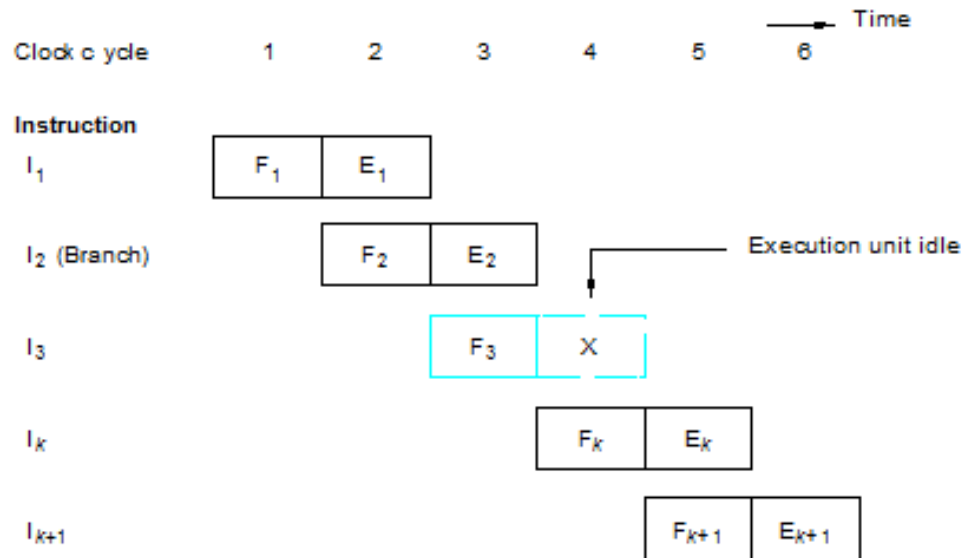
**Unconditional Branches**

Figure 8.8. An idle cycle caused by a branch instruction.

**Branch Timing**

- Branch penalty
- Reducing the penalty

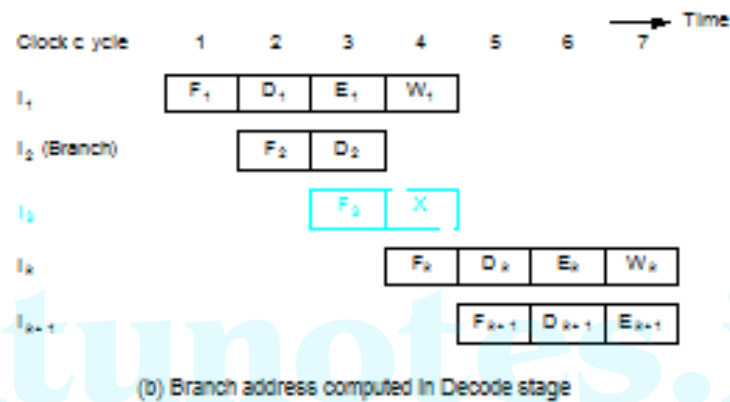
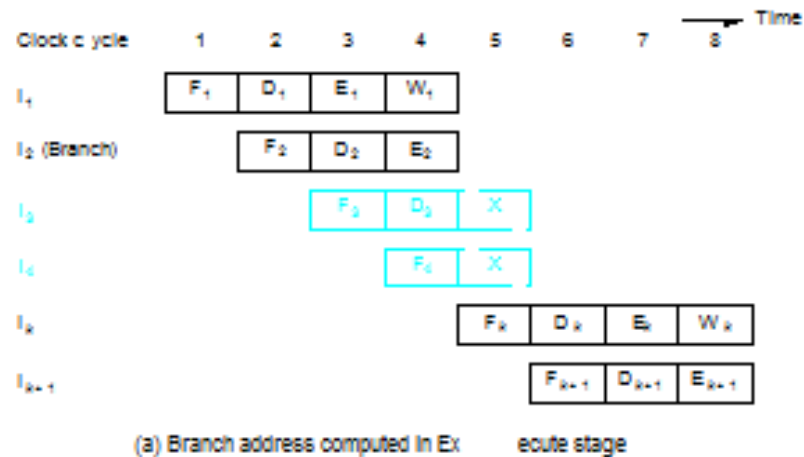


Figure 8.9. Branch timing.

### Instruction Queue and Prefetching

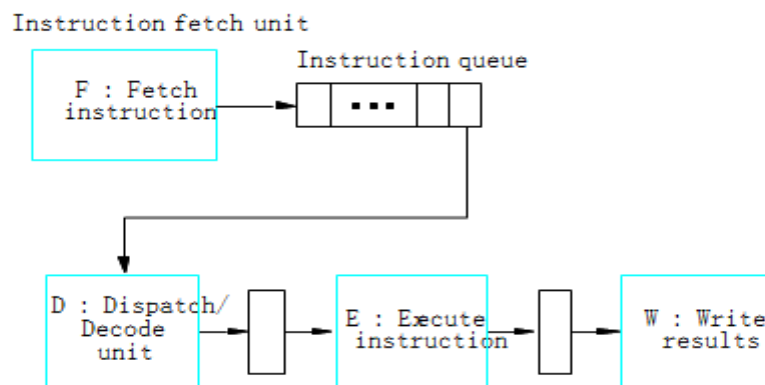


Figure 8.10. Use of an instruction queue in the hardware organization of Figure 8.2b.

**Conditional Branches**

- A conditional branch instruction introduces the added hazard caused by the dependency of the branch condition on the result of a preceding instruction.
- The decision to branch cannot be made until the execution of that instruction has been completed.
- Branch instructions represent about 20% of the dynamic instruction count of most programs.

**Delayed Branch**

- The instructions in the delay slots are always fetched. Therefore, we would like to arrange for them to be fully executed whether or not the branch is taken.
- The objective is to place useful instructions in these slots.
- The effectiveness of the delayed branch approach depends on how often it is possible to reorder instructions.

LOOP	Shift_left	R1
	Decrement	R2
	Branch=0	LOOP
NEXT	Add	R1, R3

(a) Original program loop

LOOP	Decrement	R2
	Branch=0	LOOP
	Shift_left	R1
NEXT	Add	R1, R3

(b) Reordered instructions

Figure 8.12. Reordering of instructions for a delayed branch.

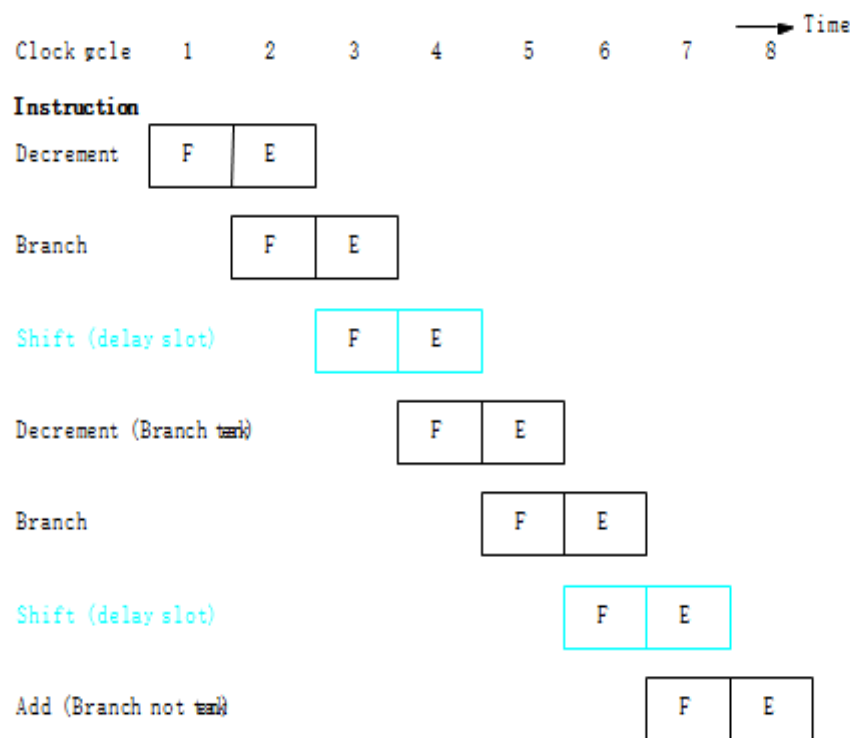


Figure 8.13. Execution timing showing the delay slot being filled during the last two passes through the loop in Figure 8.12.

### Branch Prediction

- To predict whether or not a particular branch will be taken.
- Simplest form: assume branch will not take place and continue to fetch instructions in sequential address order.
- Until the branch is evaluated, instruction execution along the predicted path must be done on a speculative basis.
- Speculative execution: instructions are executed before the processor is certain that they are in the correct execution sequence.
- Need to be careful so that no processor registers or memory locations are updated until it is confirmed that these instructions should indeed be executed.

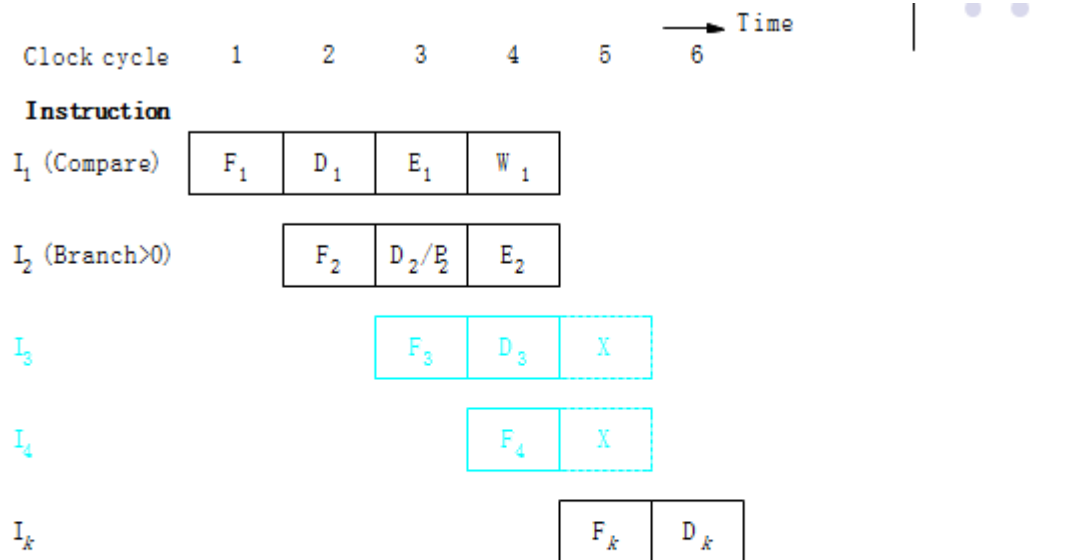
**Incorrectly Predicted Branch**

Figure 8.14. Timing when a branch decision has been incorrectly predicted as not taken.

**Branch Prediction**

- Better performance can be achieved if we arrange for some branch instructions to be predicted as taken and others as not taken.
- Use hardware to observe whether the target address is lower or higher than that of the branch instruction.
- Let compiler include a branch prediction bit.
- So far the branch prediction decision is always the same every time a given instruction is executed – static branch prediction.